

Electrical Theory

Impedance

PJM State & Member Training Dept.


By the end of this presentation the Learner should be able to:

- Identify the components of impedance in AC Circuits
- Calculate the total impedance in AC Circuits
- Identify the characteristics of Phase Angles

Components of Impedance in AC Circuits

Resistance

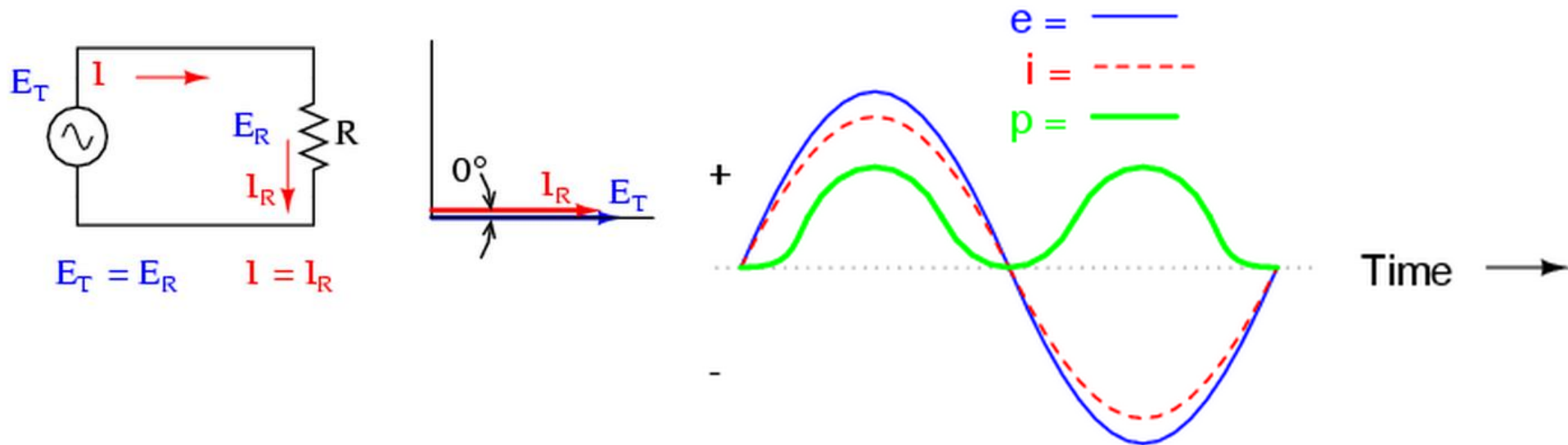- Resistance: $R = \frac{E}{I}$
- A change in frequency has no effect on resistance
- Current through a resistor and the voltage drop across the resistor are always in phase



Resistance Characteristics

- In a purely resistive AC circuit:
 - Voltage and current cycles begin and end at the same time
 - Voltage and current peak values occur at the same time
- Relationship between current and voltage for resistance in an AC circuit is the same as it is in a DC circuit
- Measured values of current and voltage are the Root Mean Square (RMS) values of these quantities
- Only resistance consumes power in a circuit

$$P = E_{RMS} I_{RMS} \cos \theta$$

Inductive Reactance Characteristics

- An inductor's basis of operation is Faraday's law of electromagnetic induction
- An inductor develops a voltage that opposes a change in current
- Does not convert electrical energy into heat energy

Inductive Reactance Characteristics

- It is the result of induced voltage in a coil by the moving magnetic field created by current flow
- Current must be changing for voltage to be induced
- An inductor allows just enough current flow to produce a voltage equal to but opposing the source voltage
- Inductive reactance (X_L) is measured in ohms and determines how much RMS current exists in an inductor for a given RMS voltage across the inductor

Inductive Reactance

- Average power and average energy used by a inductor in an AC circuit is zero
 - a) When the voltage and current product is positive, the inductor is returning energy
 - b) When the voltage and current product is negative, energy is delivered to the inductor

Inductive Reactance

- Ohm's Law and inductive reactance:

where, $E = (I)(X_L)$ $X_L = 2\pi fL$

E and I = RMS values for voltage and current




f = frequency (hertz)

L = inductance (henry)

- Increasing frequency increases inductive reactance
- As frequency increases, current changes more rapidly increasing the value of induced voltage

Inductive Reactance

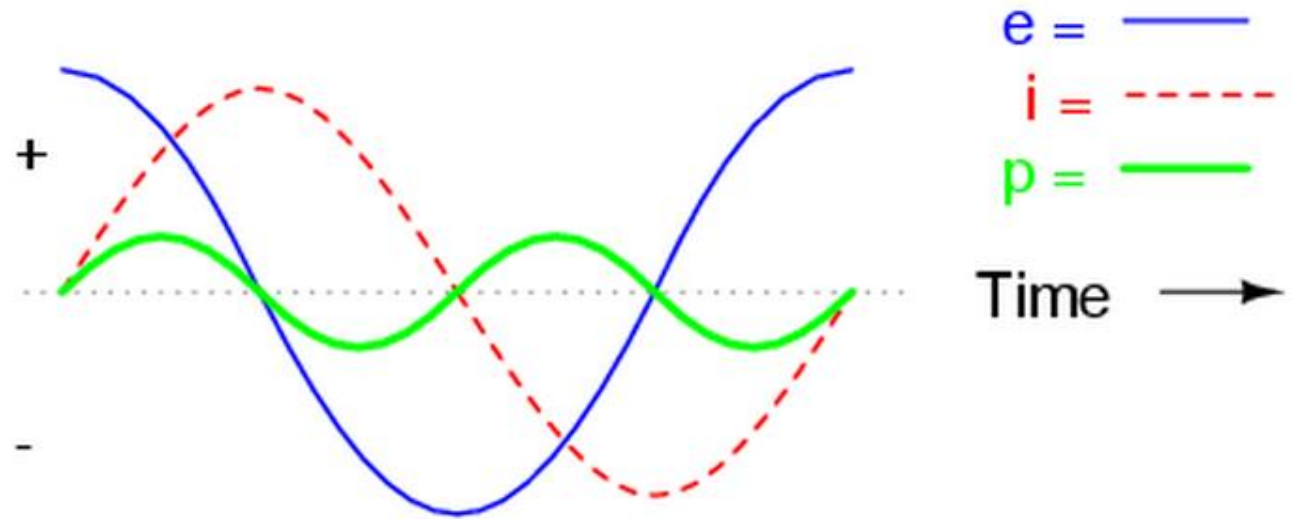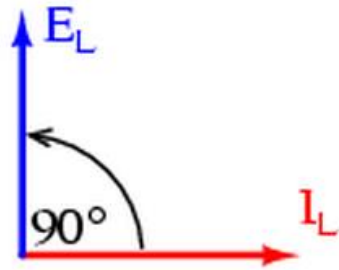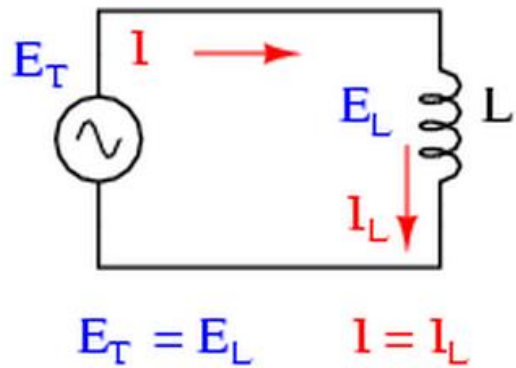In a purely inductive circuit, voltage leads the current by 90 degrees



Capacitive Reactance

- Ohm's Law and capacitive reactance: $I = \frac{E}{X_C}$ $X_C = \frac{1}{2\pi f C}$

where,

E and I = RMS values for voltage and current

f = frequency (hertz)

C = capacitance (farads)

- Increasing frequency decreases capacitive reactance
- As frequency decreases, capacitive reactance becomes infinitely large, and a capacitor provides so much opposition to the motion of charges that there is no flow of current

Capacitive Reactance Characteristics




- In an AC circuit containing a capacitor, the polarity of the voltage continually reverses switching back and forth with the electrical charges also surging back and forth
- This constitutes an alternating current with charge flowing continuously
- A capacitor controls the current in an AC circuit by storing energy that produces voltage in a capacitor
- Capacitive reactance (X_C) is measured in ohms and determines how much RMS current exists in a capacitor in response to a given RMS voltage across the capacitor

Capacitive Reactance Characteristics

- Does not convert electrical energy into heat energy
- It is the result of the capacitor storing energy that produces a voltage that opposes the source voltage and controls current
- Average power and average energy used by a capacitor in an AC circuit is zero
 - a) When the voltage and current product is positive, energy is delivered to the capacitor
 - b) When the voltage and current product is negative, the capacitor is returning energy

Capacitive Reactance

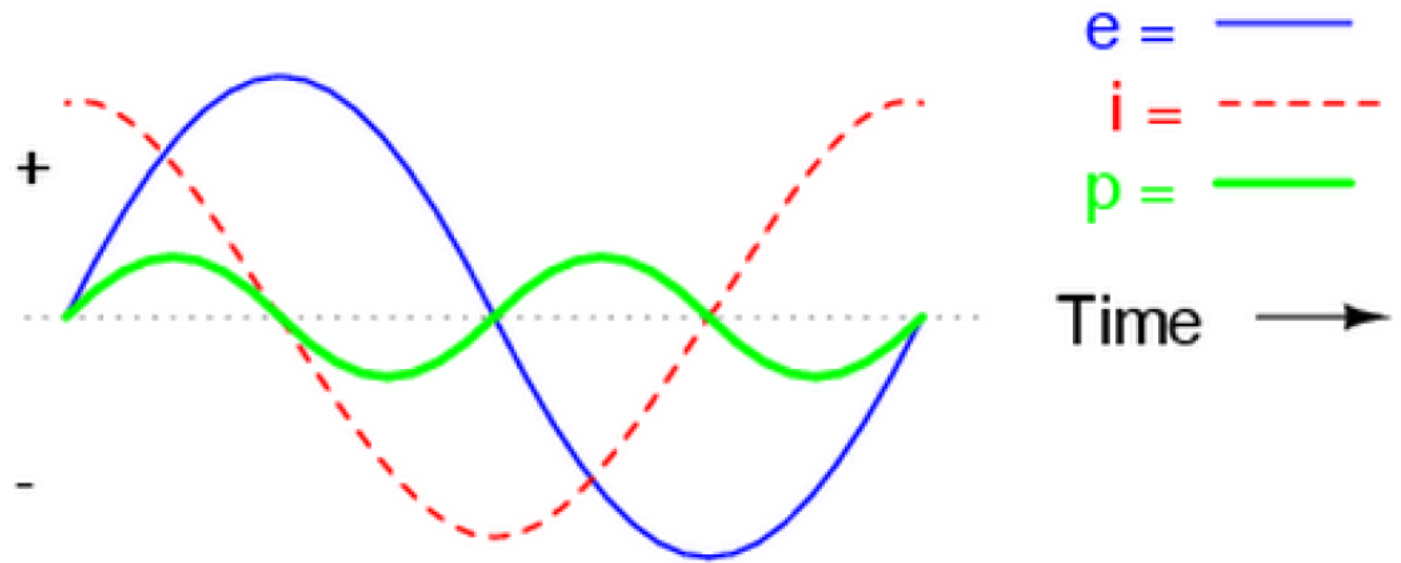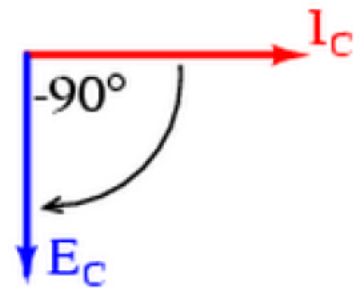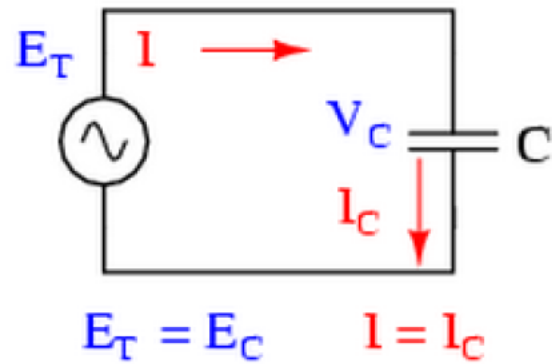- In a purely capacitive circuit, current leads the voltage by 90 degrees



Capacitive Reactance

- Capacitors are used by utilities for:
 - Voltage regulation
 - Power factor correction
 - Inductance reduction
 - Measuring devices for protection systems
 - Communications for power line carriers
 - Filters for undesirable high frequency signals

Total Impedance in AC Circuits

Total Impedance

- The impedance (Z) of an AC circuit is a complex sum of resistance (R) and net reactance ($X_L - X_C$)
- Impedance usually represented in polar form, with a magnitude and an angle ($Z \angle \theta$)
- Impedance is the total opposition to the flow of charge in an AC circuit
- A right triangle, called the impedance triangle is used to illustrate the relationship between AC resistance, reactance, and impedance

Total Impedance

- Impedance (Z) is measured in ohms and defined as: $Z = \sqrt{R^2 + X_T^2}$

Where:

$$X_T = X_L - X_C$$

R = Resistance


X_T = Total Reactance

X_L = Inductive Reactance

X_C = Capacitive Reactance

- X_L and X_C are 180° out of phase

Total Impedance

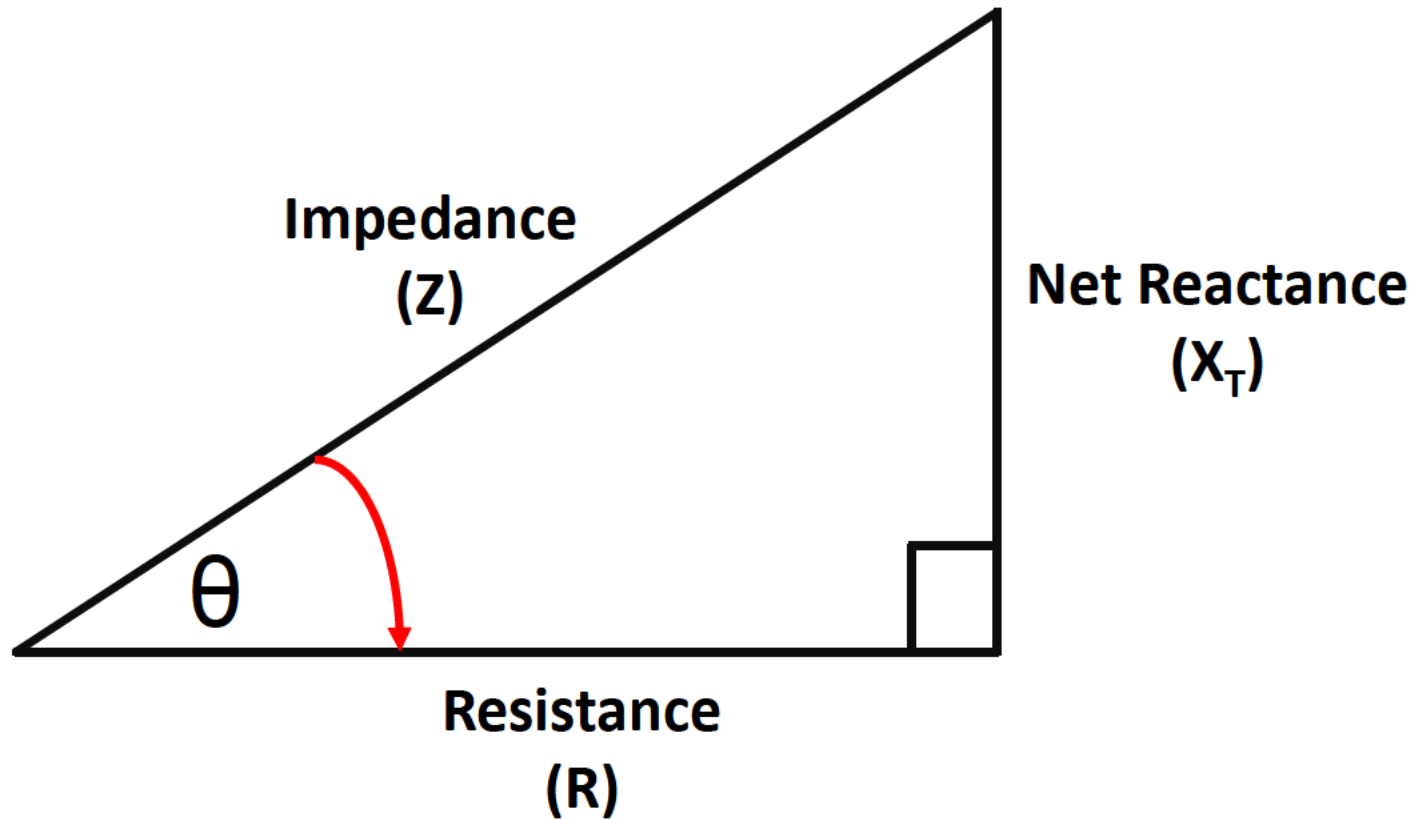

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \frac{R}{\cos \theta}$$


$$Z = \frac{X_T}{\sin \theta}$$

Total Impedance


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \frac{R}{\cos \theta}$$

$$Z = \frac{X_T}{\sin \theta}$$

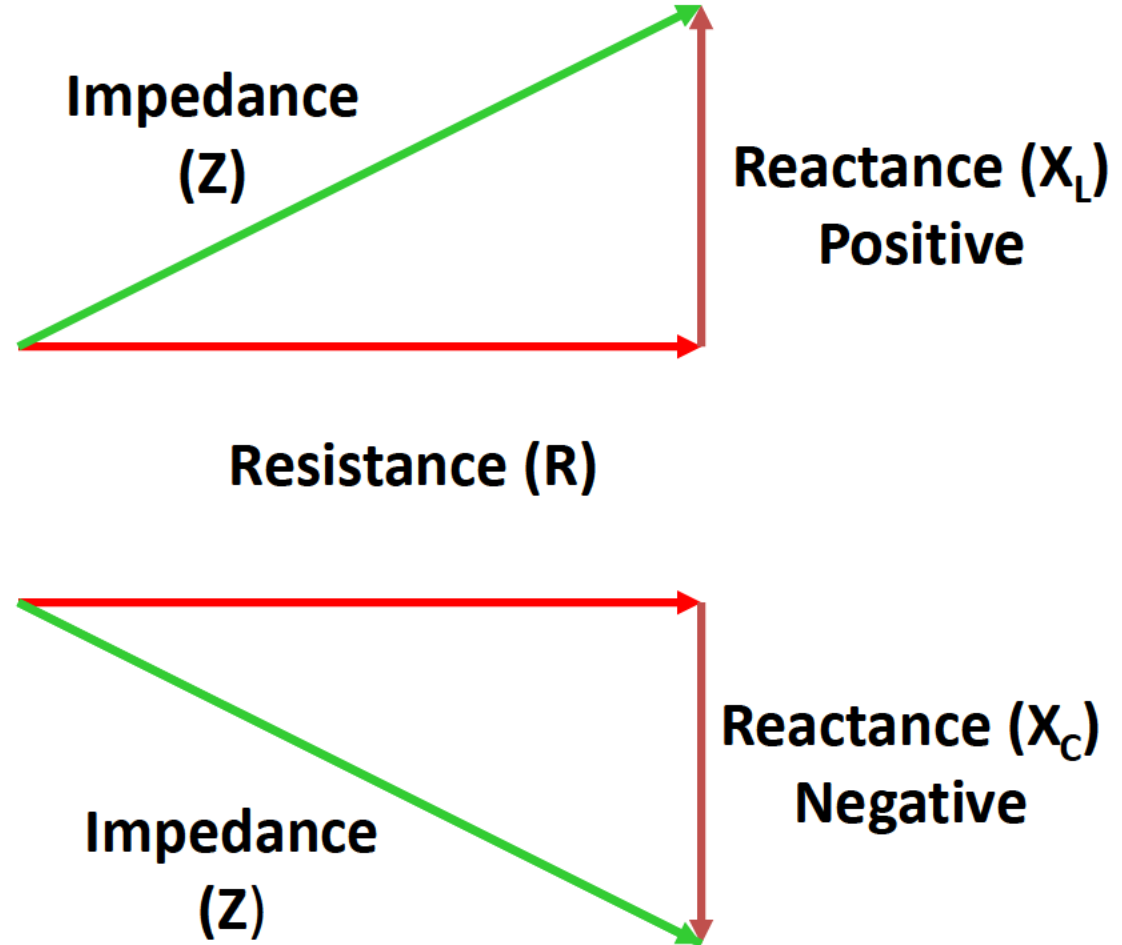

Total Impedance


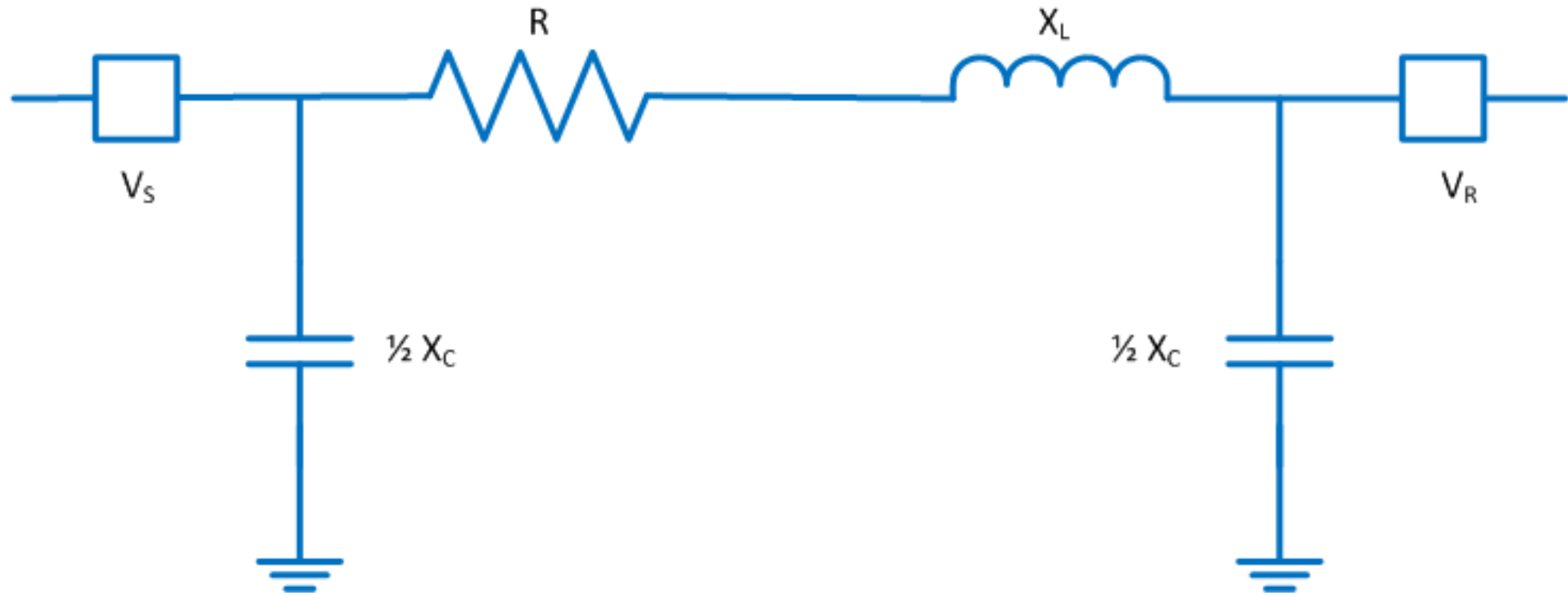


**Values will depend on a line's length, cross-sectional area,
and conductor spacing**

Phase Angles


Phase Angle

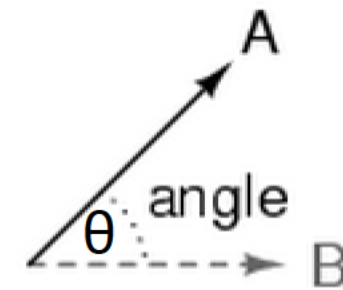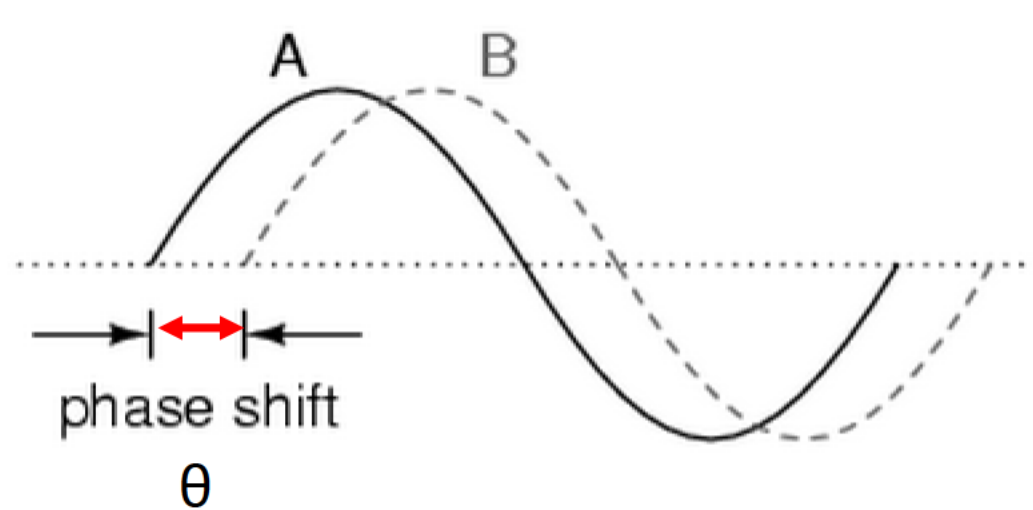- Phase angle is defined as the angular separation between two phasors
- The spacing between the zero crossings of two waveforms also illustrates the phase angle (θ) of the circuit




Phase Angle

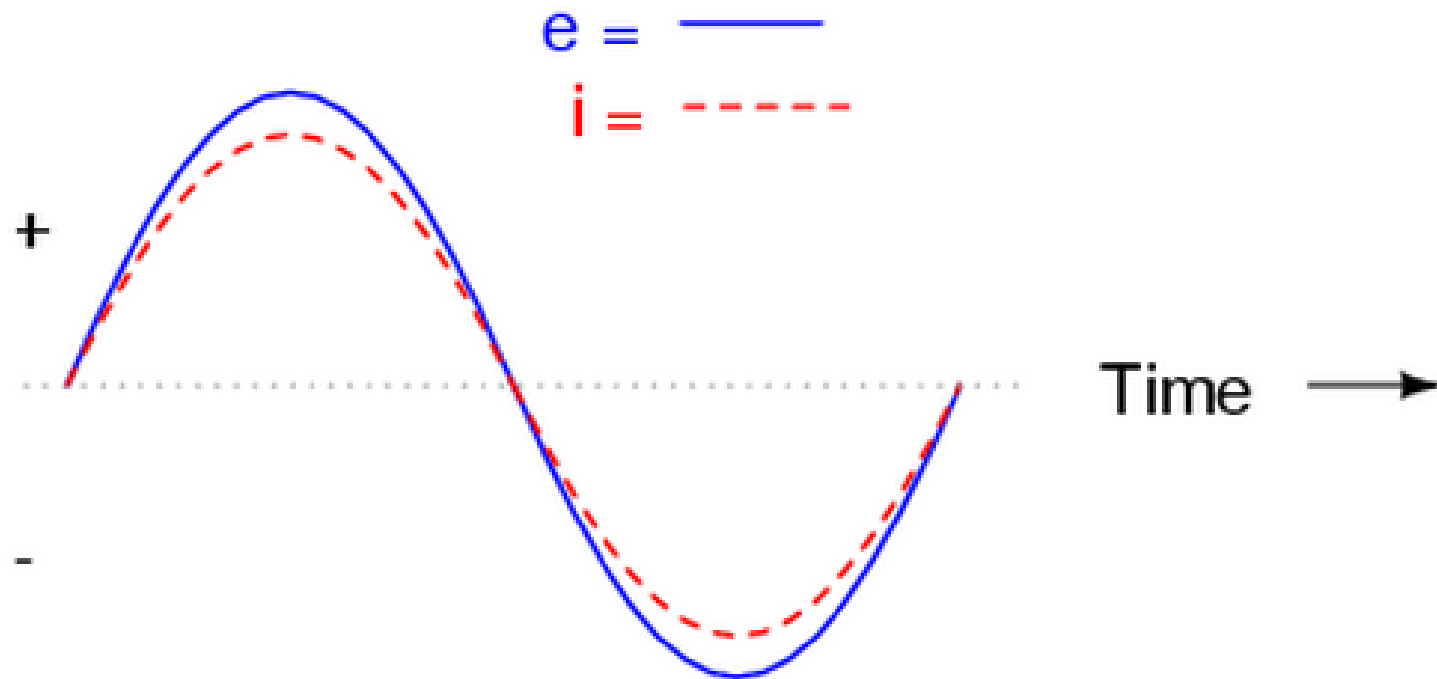- The phase angle of a circuit is directly related to the impedance of the circuit
- For a purely resistive circuit, voltage and current will be in phase, and the phase angle will be zero




Phase Angle

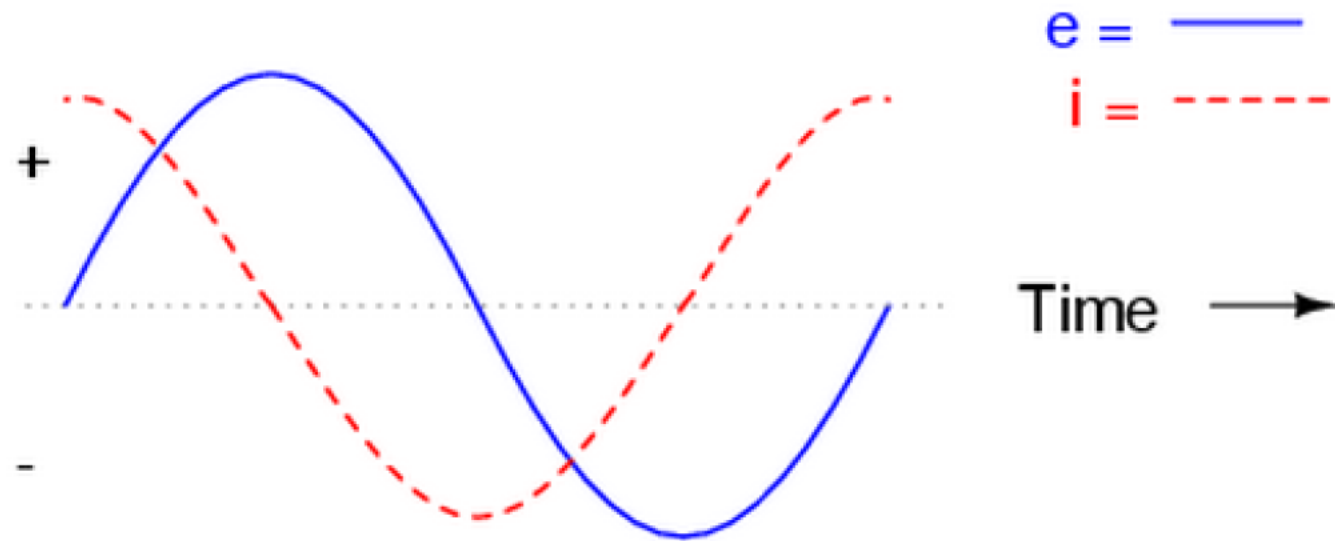- A circuit has a leading phase angle when the current wave leads the voltage wave
- This occurs when the circuit is predominantly capacitive because of the energy storage of the electric field



Phase Angle

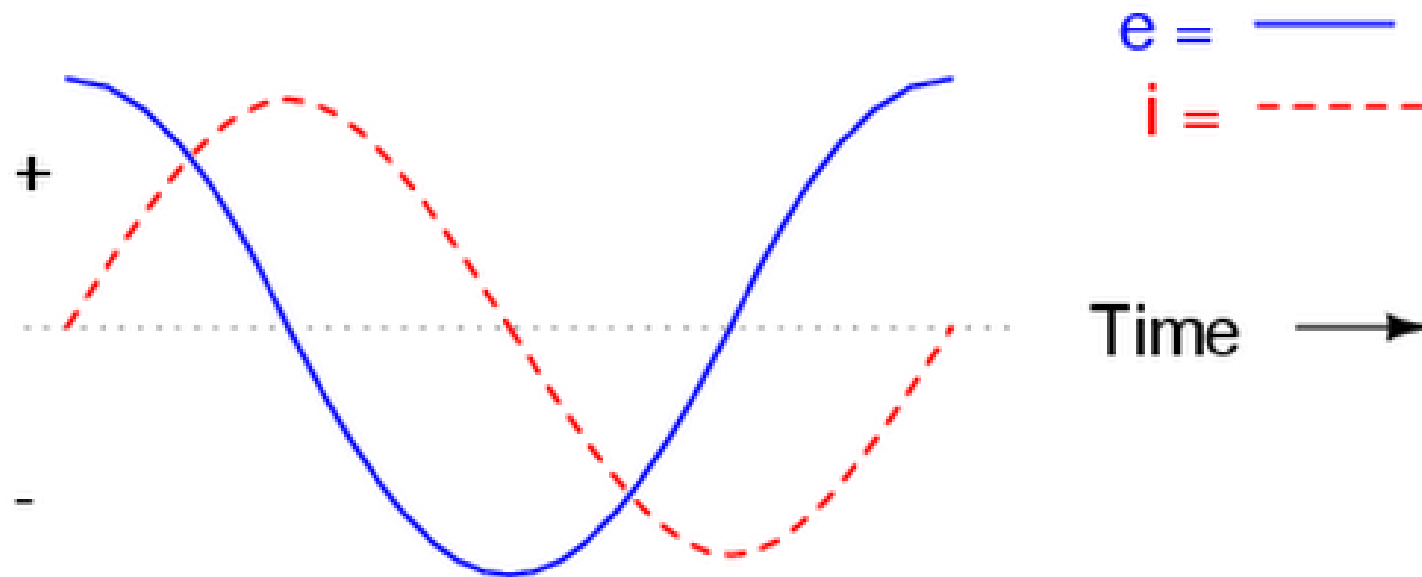- A circuit has a lagging phase angle when the current wave lags behind the voltage wave
- This occurs when the circuit is predominantly inductive because of the energy storage of the magnetic field



Questions?

PJM Client Management & Services

Telephone: (610) 666-8980

Toll Free Telephone: (866) 400-8980

Website: www.pjm.com



The Member Community is PJM's self-service portal for members to search for answers to their questions or to track and/or open cases with Client Management & Services