

Basic Electrical Theory

Power Principles and Phase Angle

PJM State & Member Training Dept.

- At the end of this presentation the learner will be able to;
 - Identify the characteristics of Sine Waves
 - Discuss the principles of AC Voltage, Current, and Phase Relations
 - Compute the Energy and Power on AC Systems
 - Identify Three-Phase Power and its configurations

Sine Waves

Sine Waves

- Generator operation is based on the principles of electromagnetic induction which states:

When a conductor moves, cuts, or passes through a magnetic field, or vice versa, a voltage is induced in the conductor


- When a generator shaft rotates, a conductor loop is forced through a magnetic field inducing a voltage

Sine Waves




- The magnitude of the induced voltage is dependant upon:
 - Strength of the magnetic field
 - Position of the conductor loop in reference to the magnetic lines of force
- As the conductor rotates through the magnetic field, the shape produced by the changing magnitude of the voltage is a sine wave
- <http://micro.magnet.fsu.edu/electromag/java/generator/ac.html>

Sine Waves

Coil Angle (θ)	0	45	90	135	180	225	270	315	360
$e = V_{\max} \sin \theta$	0	70.71	100	70.71	0	-70.71	-100	-70.71	-0

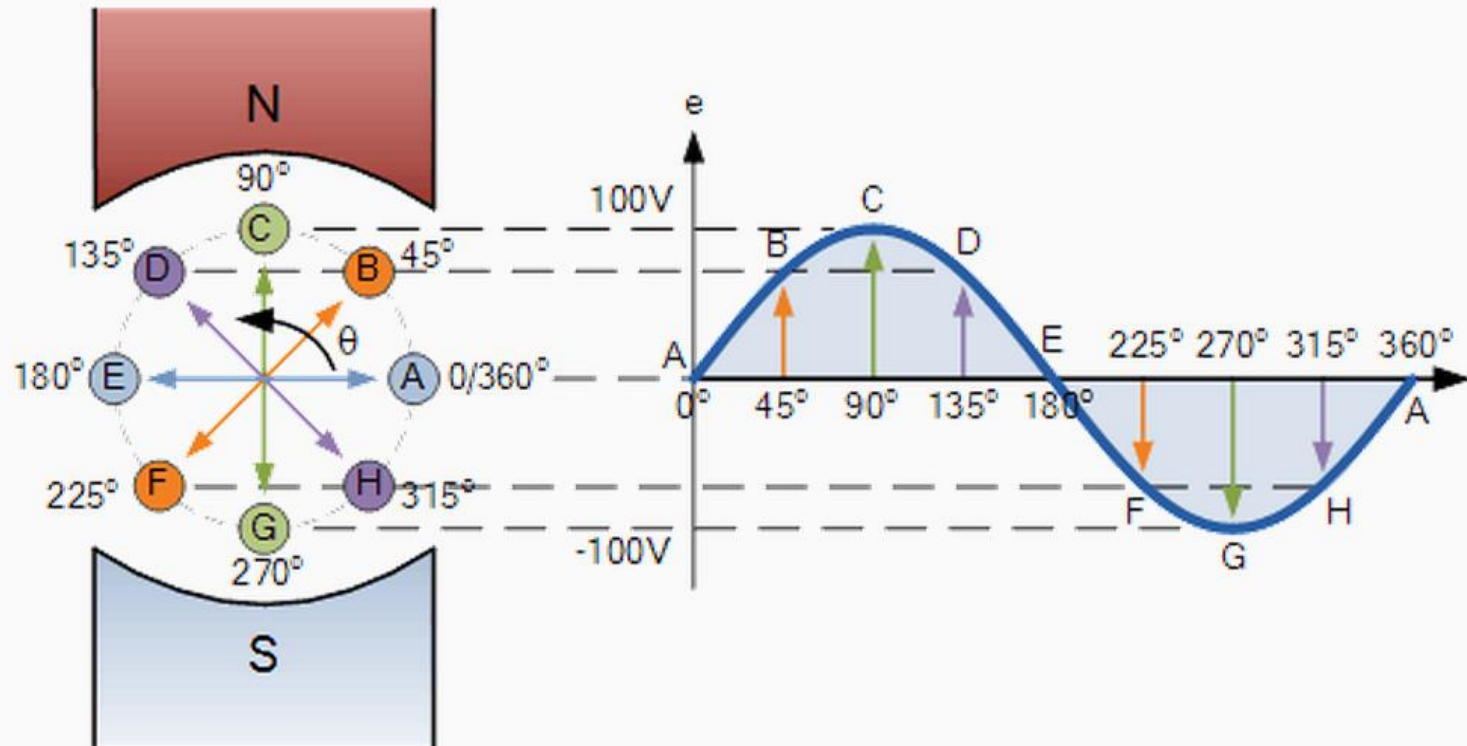

Sine Waves

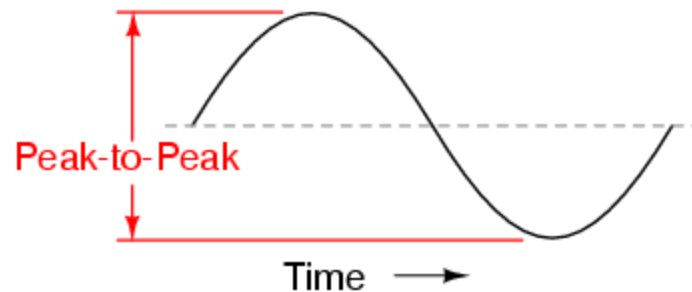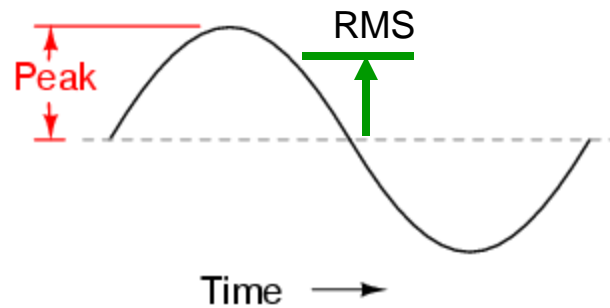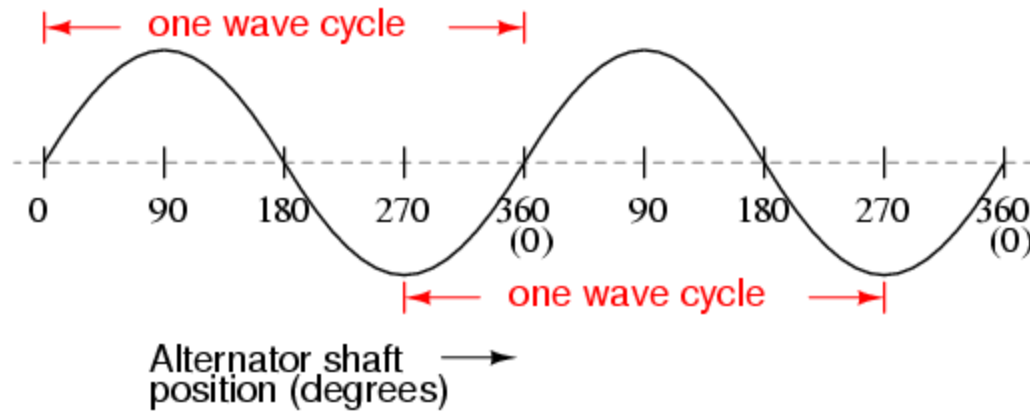

Sine Waves

- A cycle is the part of a sine wave that does not repeat or duplicate itself
- A period (T) is the time required to complete one cycle
- Frequency (f) is the rate at which cycles are produced
- Frequency is measured in hertz (Hz), One hertz equals one cycle per second

$$T = \frac{1}{f} \qquad f = \frac{1}{T}$$

$$T = \frac{1}{60 \text{ Hz}} = .0167 \text{ seconds}$$

Sine Waves

- The amplitude of a sine wave is the value of the voltage at a specific time, It can be given in either peak or peak-to-peak values
- Peak value is the waveform's maximum value and occurs twice each cycle
- Peak-to-peak value is equal to twice the peak value:

$$E_{p-p} = 2 (E_p)$$

Sine Waves

- **Root Mean Square** or the effective value is the amount of alternating current having the same heating effect in a resistive circuit as a given amount of direct current
- One ampere of AC RMS and one ampere of direct current produce the same power when flowing through equivalent circuits

$$I_{RMS} = 0.707(I_P)$$

Sine Waves

- The relationship between the peak value and the RMS value of voltage is similar;

$$E_{\text{RMS}} = 0.707 (E_p)$$

- Magnitudes of AC values are usually given in terms of effective (RMS) values

Question 1

The common 120 volt AC wall outlet means that the Root Mean Square (RMS) value of the outlet is 120 volts.

What is the maximum or peak voltage?

$$E_{\text{RMS}} = 0.707 E_{\text{P}}$$

$$E_{\text{P}} = \frac{E_{\text{RMS}}}{0.707} = \frac{120 \text{ V}}{0.707} = 169.73 \text{ V}$$

Question 2

Amtrak operates the electrical system for their railroad at 25 Hz.

What is the period of this waveform?

$$t = \frac{1}{f} = \frac{1}{25 \text{ Hz}} = 0.04 \text{ seconds}$$

Question 3

Which of the following describes the part of a waveform that does not repeat or duplicate itself?

- a) Peak
- b) Frequency
- c) Cycle
- d) RMS value

Question 4

Find the frequency and the RMS voltage values for a waveform that has a 50V peak and a time per cycle of 0.25 seconds

$$f = \frac{1}{t} = \frac{1}{0.25 \text{ seconds}} = 4 \text{ Hz}$$

$$E_{\text{RMS}} = 0.707E_{\text{P}} = (0.707)(50 \text{ V}) = 35.35 \text{ volts}$$

Question 5

A relay causes a breaker to operate to clear a line fault after 25 cycles. How long does the fault current exist before the breaker opens assuming the system is operating at 60 Hz?

$$t = \frac{1}{f} = \frac{1}{60 \text{ Hz}} = 0.0167 \text{ seconds/cycle}$$

$$(25 \text{ cycles})(0.0167 \text{ seconds/cycle}) = 0.417 \text{ seconds}$$

AC Voltage and Current

AC Voltage & Current

- Review:
 - DC current flows in only one direction at a constant magnitude
 - AC current continually changes in both magnitude and direction
 - AC current flows in one direction, then flows in the opposite direction
 - If AC current is present, there must also be alternating voltage and power
 - AC voltage produces the AC current
 - AC power is produced by the AC current and AC voltage

AC Voltage & Current

- AC voltage formula: $E = E_{\max} \sin \Theta$

where:

E = value of the induced emf (volts)


E_{\max} = maximum induced emf (volts)

Θ = angle from the reference (degrees)

- E_{\max} is also referred to as amplitude or peak voltage (E_p)

AC Voltage & Current

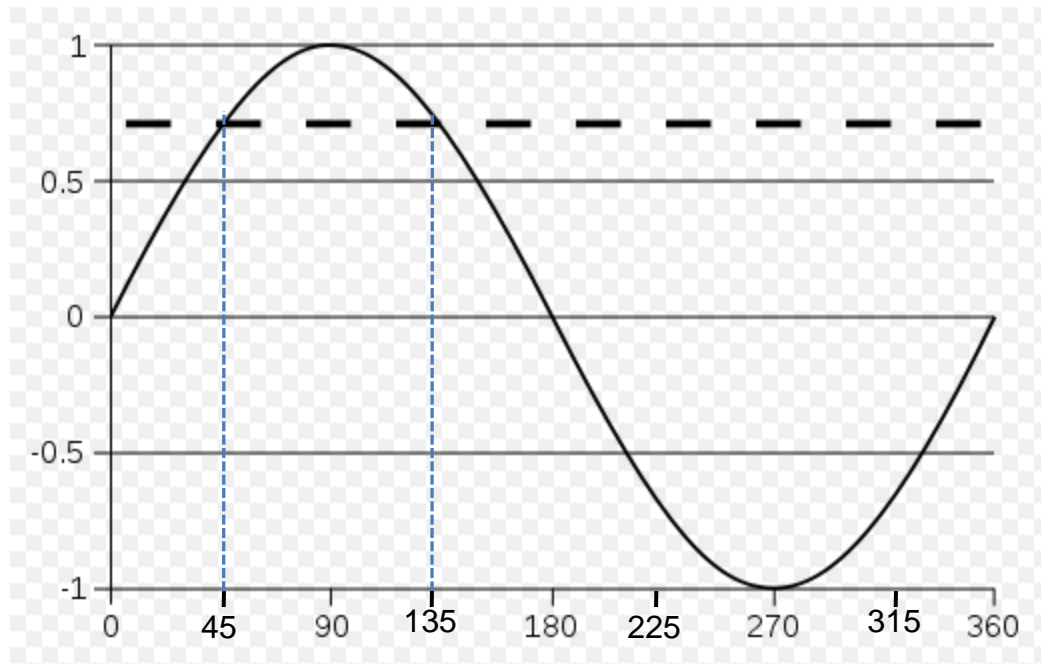- The instantaneous voltage at any given point along the sine wave is equal to: $E = E_{\max} \sin \Theta$



AC Voltage & Current

- The same equations can be used to transform current
- AC instantaneous current formula:

$$I = I_{\max} \sin \theta$$

- Rotation of the conductor in the field produces an emf, but current will not flow unless the circuit path is closed

AC Voltage & Current

- Advantages of AC power over DC power:
 - Easier to transform one AC voltage level to another
 - Efficiency of power transmission much better at higher voltages
 - AC motors are less complex than DC motors and require less maintenance (No brushes or commutators)

AC Voltage & Current

- Advantages of DC power over AC power:
 - AC losses associated with series inductance and line charging due to capacitance are eliminated
 - HVDC lines require only two power conductors rather than three required for AC facilities
 - HVDC lines can tie two AC power systems having dissimilar characteristics (50 Hz to 60 Hz)

Question 6

A stereo receiver applies a peak AC voltage of 34 volts to a speaker. The speaker behaves approximately as if it had a resistance of 8.0 ohms. Determine the (a) rms voltage, (b) rms current, and (c) average power for this circuit

$$\text{a) } E_{\text{RMS}} = 0.707 E_P = 0.707(34 \text{ V}) = 24.04 \text{ V}$$

$$\text{b) } I_{\text{RMS}} = \frac{E_{\text{RMS}}}{R} = \frac{24.04 \text{ V}}{8 \Omega} = 3 \text{ A}$$

$$\text{c) } P = IE = (3 \text{ A})(24.04 \text{ V}) = 72.2 \text{ W}$$


Phase Relations

Phase Relations

- Sine waves with the same frequency have what is termed as phase relations
- A Phase relation, or phase angle, is the angular difference between sine waves of the same frequency
- Phase angle is the portion of a cycle that has elapsed since another wave passed through a given value

Phase Relations

Sine and Cosine

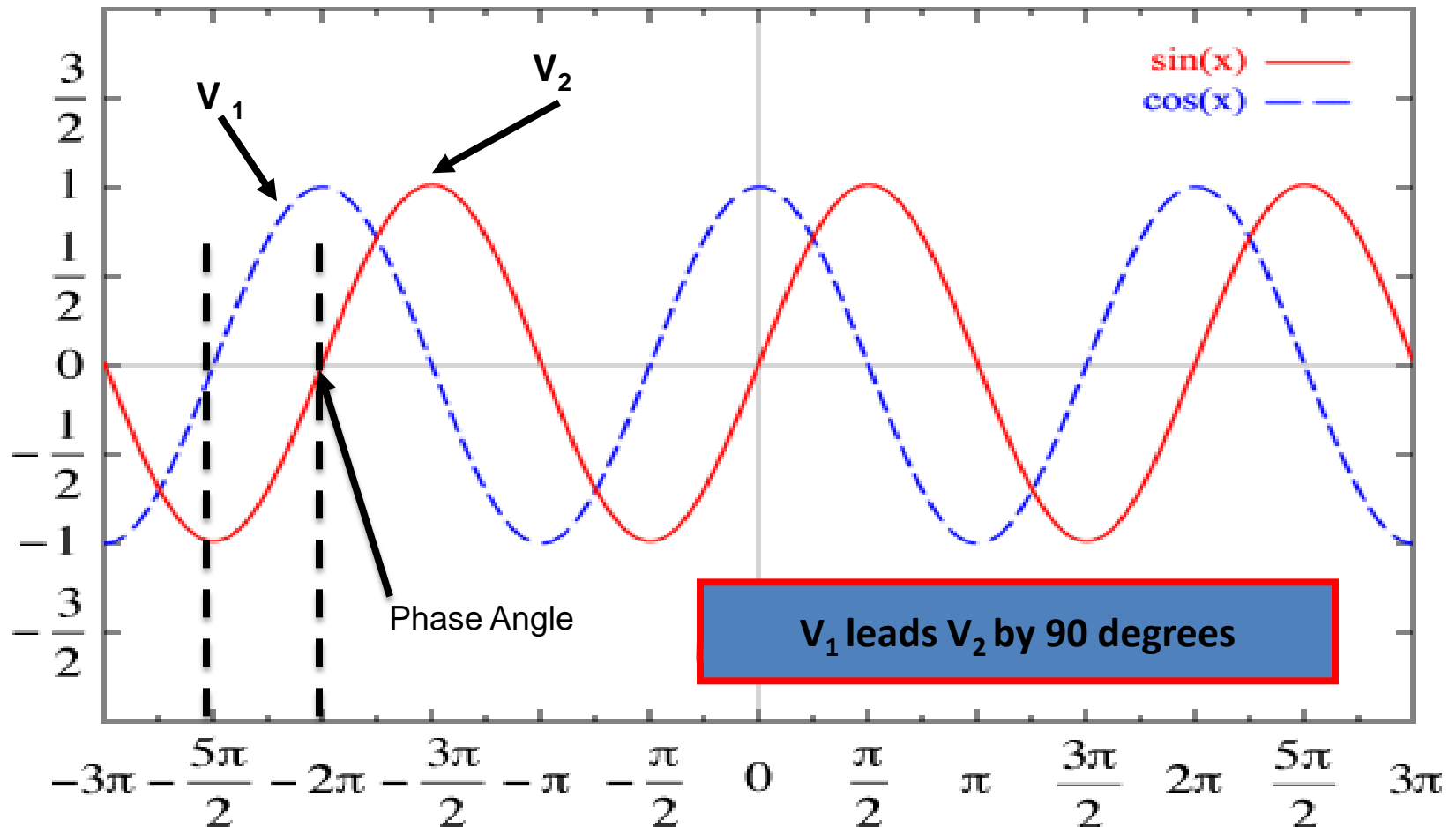

Phase Relations

- In-phase means the phase difference between two variables is equal to zero degrees
- Out-of-phase means that the phase difference between two variables is not zero degrees
- Phase difference only applies to waveforms that have the same frequency (each waveform should complete one cycle in the same amount of time)
- Angle θ is used when comparing the phase angle difference between voltage and current
- Angle δ is used when comparing the phase angle difference between two voltage curves or two current curves


Review

- Are the waves both the same frequency?

Yes

- Does the voltage lead or lag the current?

Voltage leads the current

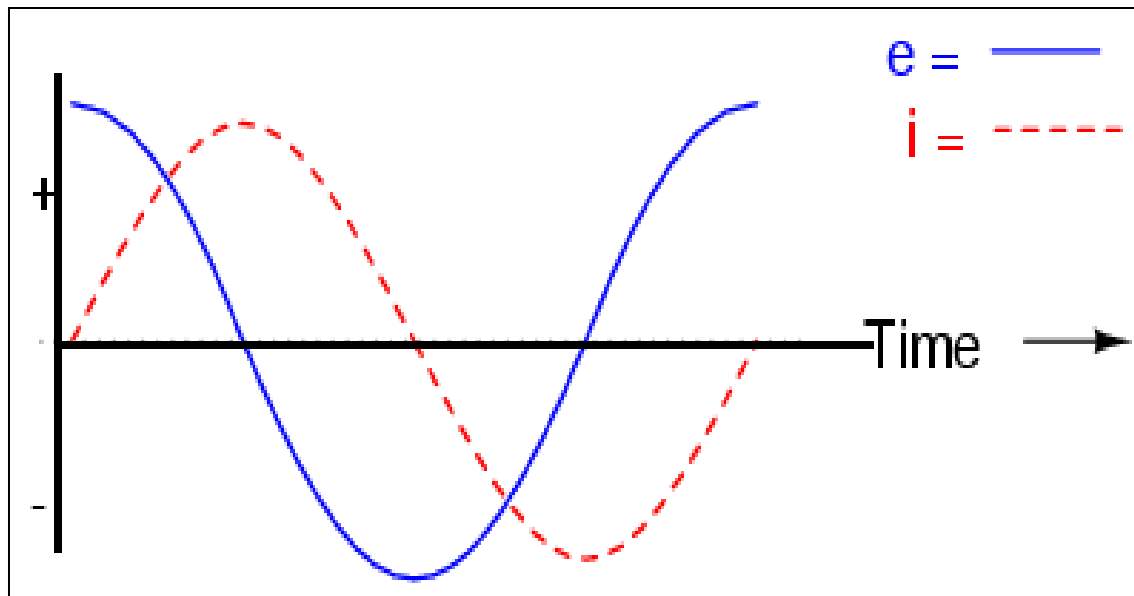

Energy & Power AC Systems

Energy & Power

- The power that flows in a power system is composed of active and reactive power. Both components are necessary to serve customer loads
- Power is the rate of performing work
- Power is also the rate at which energy is used or dissipated
- The measure of electricity's ability to perform work is the **Watt**

AC and DC Power

- For a DC circuit, the power consumed is the sum of the I^2R heating in the resistors
 - Power is equal to the source power
- For an AC circuit, the power consumed is also the sum of the I^2R heating in the resistors
 - The power consumed is not always equal to the source power because of the capacitance and inductance in the circuit
- Power consumption always refers to the I^2R heating in the resistors, reactance consumes no power

AC and DC Power

- When an amount of positive charge (q) moves from a higher potential to a lower potential, its potential energy decreases (voltage potential)

$$P = \frac{\text{Change in energy}}{\text{Time interval}} \times \text{Voltage}$$

- The change in energy per unit of time is the current (I) in the device

AC and DC Power

- When an electric charge flows from point A to point B in a circuit, leading to a current (I), and the voltage between the points is (E), the electric power associated with this current and voltage is:

$$P = EI$$

- The charge can either lose or gain electric potential energy and must be accompanied by a transfer of energy to some other form (conservation of energy)

Real Power

- Many devices are essentially resistors that become hot when provided with sufficient electric power
- The power consumed by the resistance of a circuit is called “Real” or “Active” power
- Real power is the useful or working energy

$$P = EI$$

$$P = I^2R$$

$$P = \frac{E^2}{R}$$

- Real Power (P) is expressed in Watts

Question 7

What is the power delivered to an iron that has a resistance of 24 ohms which is plugged into a 120 volt outlet?

$$P = \frac{E^2}{R} = \frac{120 \text{ V}^2}{24 \Omega} = 600 \text{ W}$$

Real Power

- Monthly electric bills specify the cost of energy consumed during a month
- Energy is the product of power and time, and is computed by expressing power in kilowatts (kW) and time in hours
- Energy consumption commonly uses the units of kilowatt-hour (kWh)

Electric Energy

- Electric energy is used or produced when electric power is applied over a period of time

$$E_n = Pt$$

where,

E_n = energy in watthours

P = power in watts

t = time in hours

Question 8

What is the energy consumed by a 100 watt light bulb in 5 hours?

$$E_n = Pt = (100 \text{ W})(5 \text{ h}) = 500 \text{ Wh} = .5\text{kWh}$$

Question 9

If you used an average power of 1,440 watts for 30 days, (a) what would your energy consumption be, and (b) at a cost of \$0.12 per kWh, what would your monthly bill be?

a) $E_n = Pt = (1440 \text{ W})(30 \text{ days})(24 \text{ Hrs}) = 1036.8 \text{ kWh}$

b) $\text{Cost} = (1036.8 \text{ kWh})(\$0.12) = \$124.42$

Power in Resistive Circuits

- In a resistive circuit, current and voltage are in phase
- Active power is the rate used to perform work such as lighting a room, heating a building or turning a motor shaft
- In a generating station, more fuel must be added to the prime mover to increase the active power output
- In a transmission system, when power in a resistance is dissipated as heat (I^2R), this is considered a loss
- The general equation for real power in all types of circuits is:

$$P = EI \cos \Theta$$

Question 10

An AC circuit is supplied by a 120 volt source and contains a resistance of 20 ohms. If this is a purely resistive circuit, what is the energy consumed in 10 hours?

$$P = \frac{E^2}{R} = \frac{120 \text{ V}^2}{20 \Omega} = 720 \text{ W}$$

$$E_n = Pt = (720 \text{ W})(10 \text{ hrs}) = 7.2 \text{ kWh}$$

Reactive Power

- Reactance in an AC circuit causes a phase shift between current and voltage
- If a circuit contains only inductance, or only capacitance, a maximum phase shift of 90° occurs between the current and voltage
- Most circuits have a combination of resistance and reactance resulting in a phase shift of less than 90°
- This combination of resistance and reactance is referred to as **Impedance (Z)**

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Reactive Power


- **Reactive Power (Q)** is used to support the magnetic and electric fields found in inductive and capacitive loads
- Reactive Power is measured in volt amperes reactive (VARs)
- Unlike resistors, which consume power, inductors and capacitors store and release energy but do not consume power
- In order to calculate power in a circuit containing both real and reactive power, we must use vectors and right triangle relationships

Question 11

What is the real power being used by a circuit with a 120 volt source and a 5 ohm resistance and an inductive reactance of 4 ohms?

$$\theta = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{4}{5} = \tan^{-1}(0.8) = 38.66^\circ$$
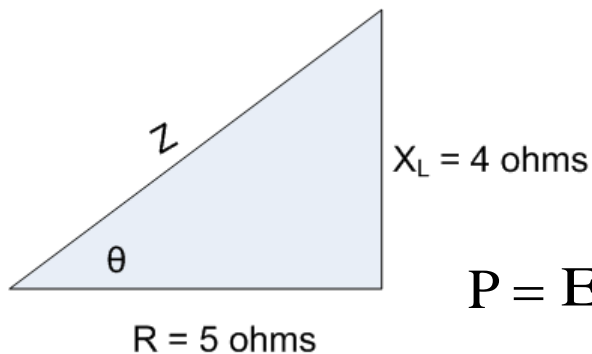
$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{5^2 + 4^2} = \sqrt{41} = 6.4 \Omega$$



$$I = \frac{E}{Z} = \frac{120 \text{ V}}{6.4 \Omega} = 18.74 \text{ A}$$

$$P = EI \cos \theta = (120 \text{ V})(18.74 \text{ A}) \cos 38.66^\circ = 1756.1 \text{ W}$$

Question 12

In the previous question, if the inductive reactance is removed from the circuit, how much real power is absorbed?

$$P = \frac{E^2}{R} = \frac{120 \text{ V}^2}{5 \Omega} = 2880 \text{ W} = 2.88 \text{ kW}$$

Apparent Power

- **Apparent Power (S)** is the power that appears to be present when voltage and current are measured separately regardless of the phase angle
- Apparent Power is the product of voltage and current

$$S = VI = \text{VoltAmperes (VA)}$$

- Real power does not equal apparent power if a circuit contains both resistance and reactance
- Real power and apparent power differ by cosine θ

Power Factor

- Power Factor (PF) is the ratio of real power to apparent power:

$$PF = \cos \theta = \frac{P}{S} = \frac{\text{Watts}}{\text{Volt Amps}}$$

- Power Factor indicates the amount of apparent power (total current and voltage) that is actually doing the work or producing the real power
- Power Factor can be any value between 0 and 1

Power Factor

- If real power equals apparent power, voltage and current are in-phase, and the resulting power factor is 1
- If real power does not equal apparent power, and voltage and current are out-of-phase by 90° , the power factor is 0
- If real power does not equal apparent power, and voltage and current are out-of-phase between 0° and 90° , power factor will be between 0 and 1

Power Factor


- Why is power factor so important?
 - a) High power factor enables motors and other equipment to provide their rated power, without drawing excess current
 - b) Electric energy transfer is more efficient with higher power factors. The power system can transmit and distribute more real power, without having to increase current-carrying capabilities of utility equipment

Question 13

Suppose a utility sells energy to (2) different manufacturers which are located equidistant from the substation. Company A utilizes motor load and operates at a power factor of 60%. Company B uses mostly resistive load and operates at a power factor of 97%. Both receive power at a voltage of 4700 volts, and both require the same real power of 2 megawatts

How does their power factor affect the current carrying capability of the utility's conductors?


Question 13

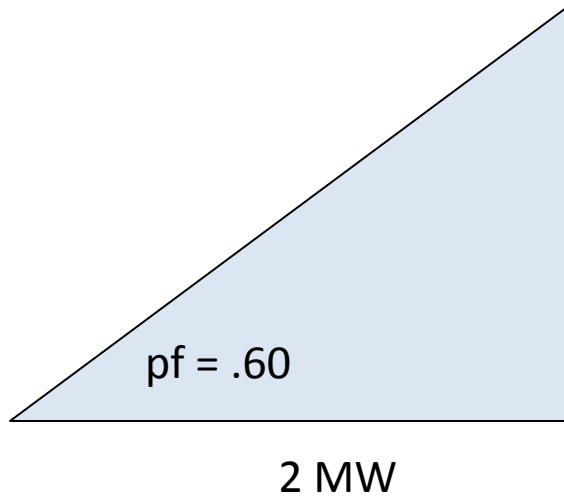

Company A

$$S = \frac{P}{\cos\theta} = \frac{2 \text{ MW}}{.6} = 3.33 \text{ MVA}$$
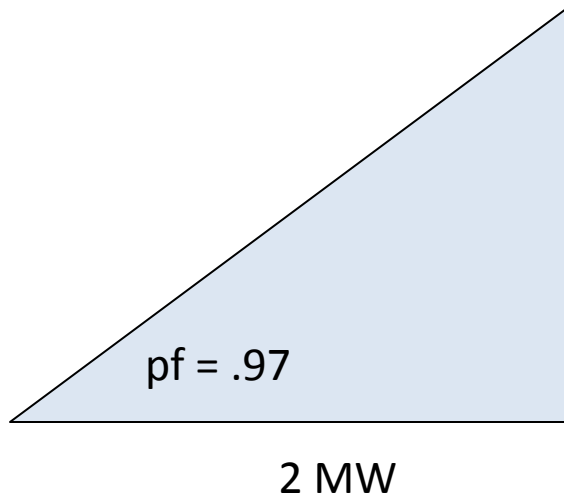
$$I = \frac{S}{E} = \frac{3.33 \text{ MVA}}{4700 \text{ V}} = 708.5 \text{ A}$$




Company B

$$S = \frac{P}{\cos\theta} = \frac{2 \text{ MW}}{.97} = 2.06 \text{ MVA}$$

$$I = \frac{S}{E} = \frac{2.06 \text{ MVA}}{4700 \text{ V}} = 438.3 \text{ A}$$


Power Triangle

$$MVA^2 = MW^2 + MVAR^2$$

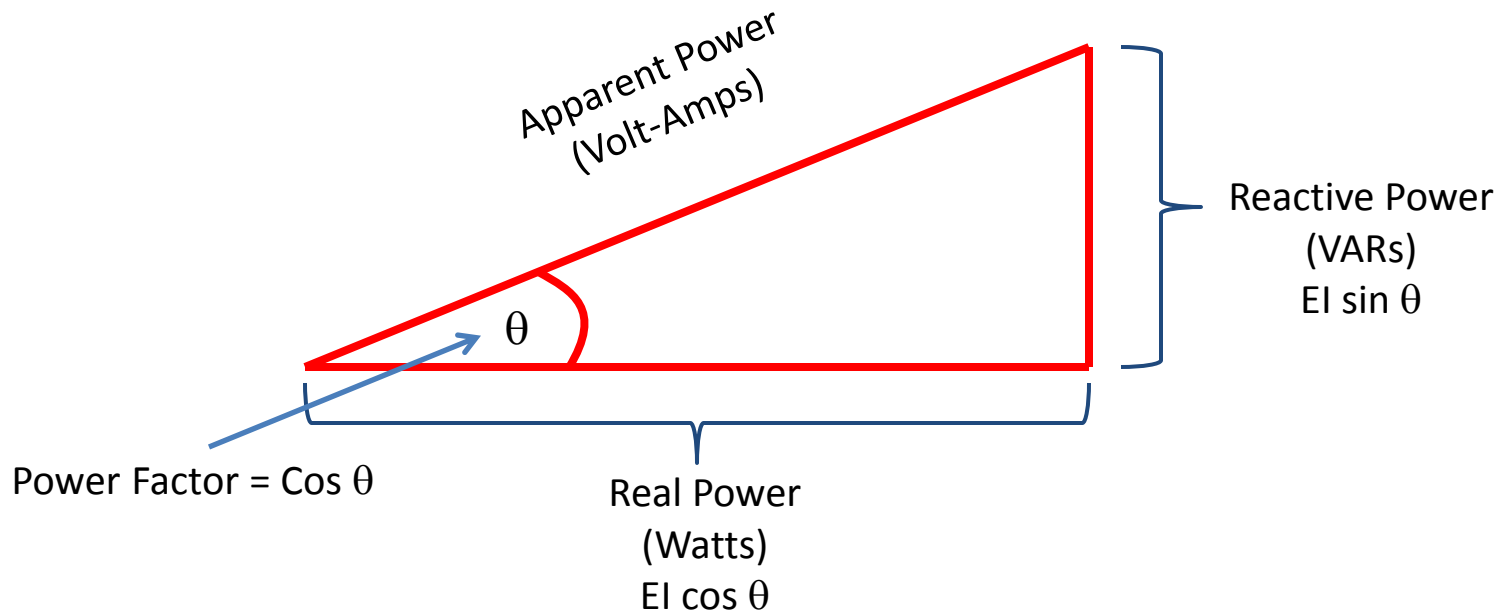

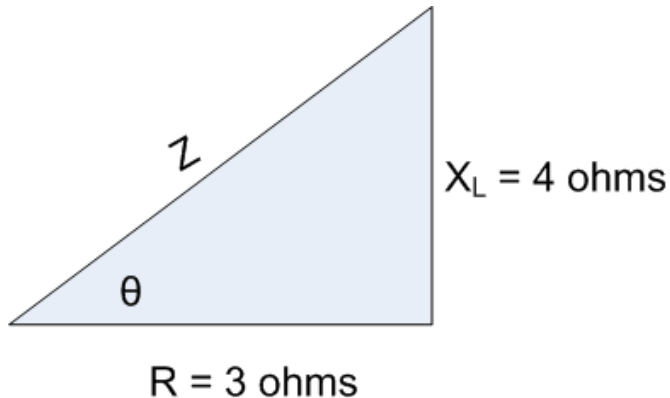Question 14

Find the actual and reactive power of a series RL circuit containing a resistance of 3 ohms, an inductive reactance of 4 ohms, and a source voltage of 220 volts



$$Z = \sqrt{3^2 + 4^2} = \sqrt{25} = 5 \Omega$$

$$I = \frac{E}{Z} = \frac{220 \text{ V}}{5 \Omega} = 44 \text{ A}$$


$$\theta = \cos^{-1} \frac{3}{5} = \cos^{-1}(0.6) = 53.13^\circ$$

$$P = EI \cos \theta = (220 \text{ V})(44 \text{ A}) \cos 53.13^\circ = 5808 \text{ Watts}$$

$$Q = EI \sin \theta = (220 \text{ V})(44 \text{ A}) \sin 53.13^\circ = 7743 \text{ VARs}$$

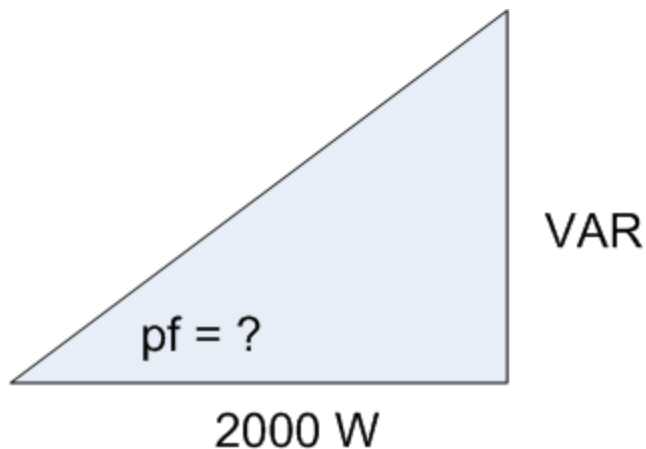Question 15

A circuit contains a 120 volt source. The current through the circuit is 30 amps lagging. The real power consumed by the circuit is 2000 watts. Find the (a) power factor and (b) the reactive power of the circuit



$$S = EA = (120 \text{ V})(30 \text{ A}) = 3600 \text{ VA}$$

$$\text{pf} = \frac{W}{EA} = \frac{2000 \text{ W}}{3600 \text{ VA}} = 0.56$$

$$\text{VARs} = \sqrt{\text{VA}^2 - W^2} = \sqrt{3600^2 - 2000^2} = 2993.33 \text{ VARs}$$

Question 16

For a series RCL circuit, the resistance, capacitance, and inductance are $R = 148$ ohms, $C = 150$ microfarads, and $L = 35.7$ millihenries. The generator has a frequency of 512 Hz and a rms voltage of 35 volts. Find the a) rms voltage across each circuit element, and b) the average electric power delivered by the generator

Question 16

$$\text{A) } X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(512 \text{ Hz})(.00015 \text{ F})} = 2.07 \Omega$$

$$X_L = 2\pi fL = 2\pi(512 \text{ Hz})(.0357 \text{ H}) = 114.85 \Omega$$

$$X_T = X_L - X_C = 114.85 \Omega - 2.07 \Omega = 112.78 \Omega$$

$$Z = \sqrt{R^2 + X_T^2} = \sqrt{148^2 + 112.78^2} = \sqrt{34623.33} = 186.07 \Omega$$

$$I = \frac{E}{Z} = \frac{25 \text{ V}}{186.07 \Omega} = 0.134 \text{ A}$$

$$\text{B) } \theta = \cos^{-1} \frac{R}{Z} = \cos^{-1} \frac{148 \Omega}{186.07 \Omega} = \cos^{-1}(.795) = 37.31^\circ$$

$$P = EI \cos \theta = (25 \text{ V})(0.134 \text{ A}) \cos 37.31^\circ = 2.66 \text{ W}$$

$$V_R = IR = (0.134 \text{ A})(148 \Omega) = 19.83 \text{ V}$$

$$V_L = IX_L = (0.134 \text{ A})(114.85 \Omega) = 15.39 \text{ V}$$

$$V_C = IX_C = (0.134 \text{ A})(2.07 \Omega) = 0.277 \text{ V}$$

LabVolt Exercises



- Do LabVolt exercise 5.1

Three-Phase Power

Three-Phase Power

- A system is balanced when the impedances in a three-phase system are identical in magnitude and phase
- Voltage, line current, real power, apparent power, reactive power, and power factor are identical in a balanced system for all three phases
- An AC generator produces three evenly-spaced sine wave voltages, each with a phase angle difference of 120°
- Three conductors or phases transmit the energy, and each phase carries its own phase current


Three-Phase Power

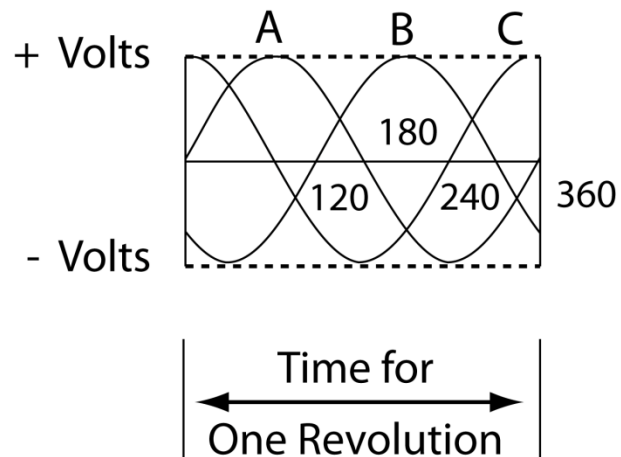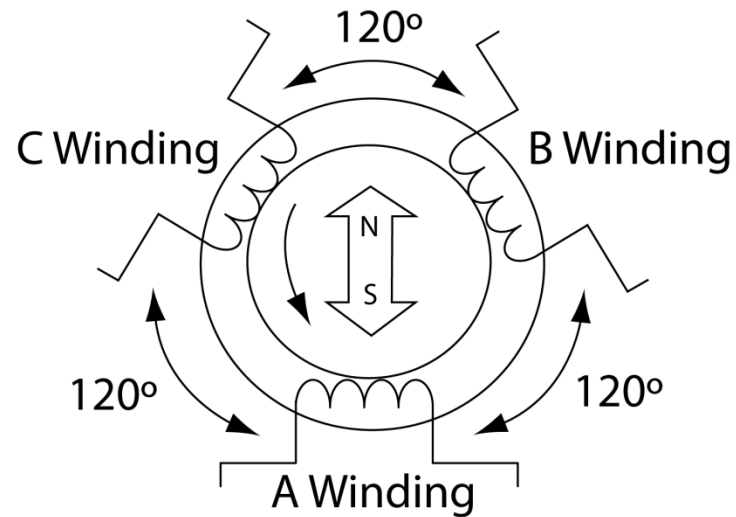

Three-Phase Power

- Utilities use three-phase systems because:
 - Cost of a three-phase transmission line is less than a single-phase line
 - A three-phase system provides a more constant load on the generator (At least two phases are providing current and power at any instant) allowing smoother operation


Three-Phase Power

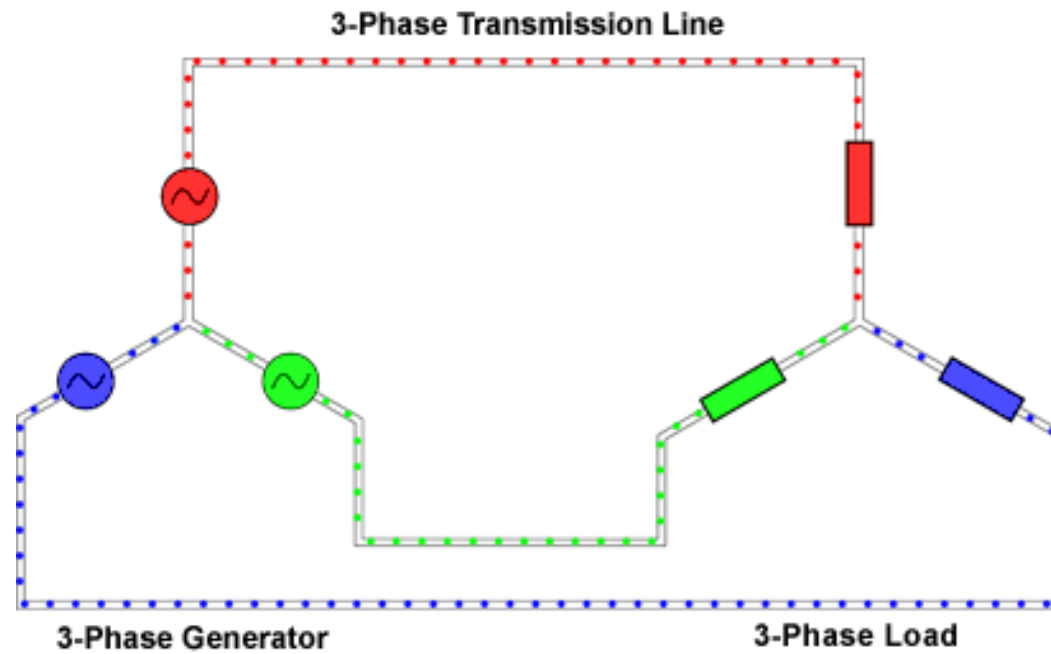

Three-Phase Power

- In a three-phase system, there are two ways to specify voltage:
 - Phase Voltage (Line-to-Ground)
 - Line Voltage (Line-to-Line)
- In a three-phase system, there are two basic types of winding connections:
 - Delta connection
 - Wye connection

Wye Connection

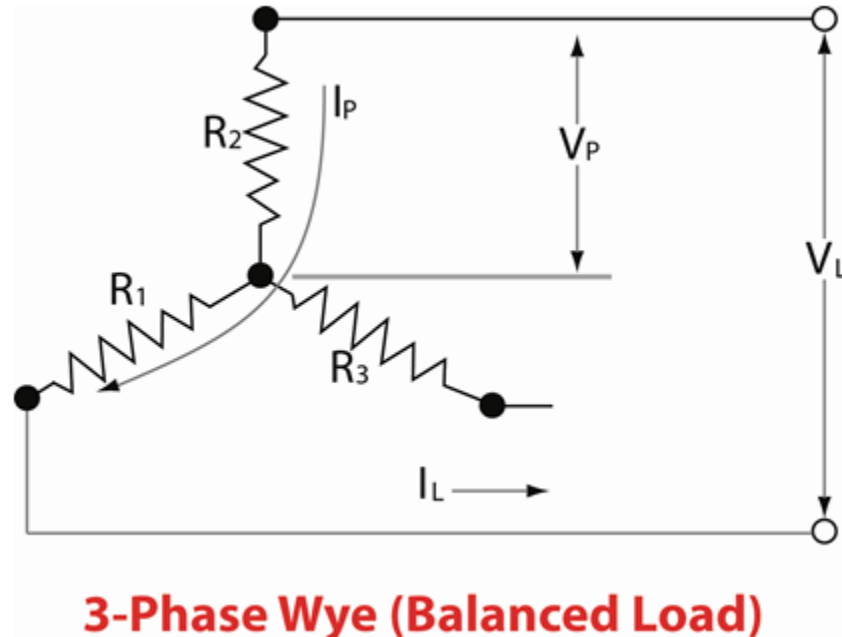

$$I_P = I_L$$

$$E_P = E_L / 1.73$$

$$W_{WYE} = E_L^2 / R = 3(E_P) / R$$

$$W_{WYE} = 1.73 E_L I_L$$

Wye Connection

- Coils are connected together at a common or neutral point (one wire for each voltage and a neutral)
- Line voltages are 120° out of phase with each other
- Line currents equal Phase currents

$$I_L = I_P$$

- Line voltages do not equal Phase voltages
- Voltage between any two lines is the result of two phase voltages being 120 degrees out of phase

$$E_L = E_P(1.732)$$

$$208\text{ V} = (120\text{ V})(1.732)$$

Question 17

A three-phase generator has a phase voltage of 120 volts at 0 degrees and supplies a wye connected load having an impedance of 50 ohms at 25 degrees per phase. Calculate the (a) line voltage, (b) phase current, and (c) line current

$$\text{a) } E_L = E_P(1.732) = 120(1.732) = 207.84 \text{ volts}$$

$$\text{b) } I_P = E_P / Z_P = \frac{120}{50 \angle 25^\circ} = 2.4 \angle -25^\circ$$

$$\text{c) } I_P = I_L = 2.4 \text{ A } \angle -25^\circ$$


$$\text{Proof - } \frac{V_L^2}{R} = W_{\text{wye}} = 1.73 (E_L)(I_L)$$

$$E_L^2 = 1.73 (E_L)(I_L)(R)$$

$$E_L = 1.73 (I_L)(R)$$

$$I_L = \frac{E_L}{1.73 (R)} = \frac{207.84}{(1.73)50 \angle 25^\circ} = 2.4 \angle -25^\circ$$

Delta Connection

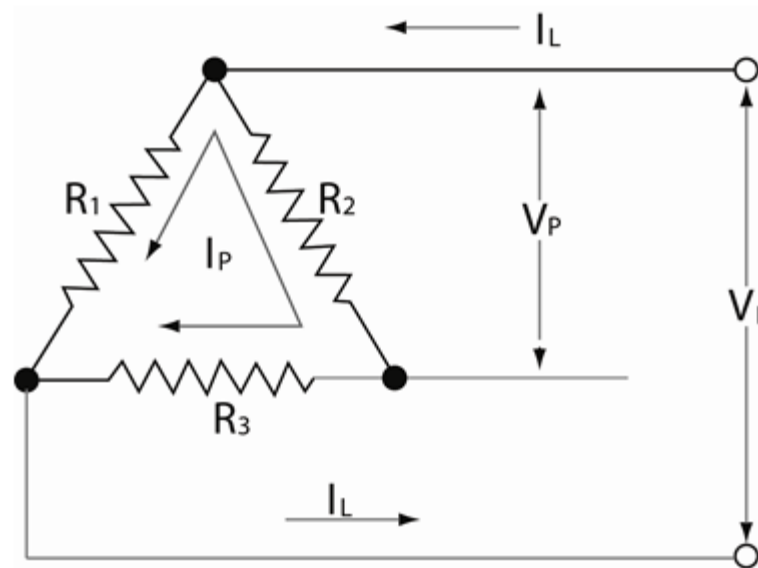

3-Phase Delta (Balanced Load)

$$I_P = I_L / 1.73$$

$$E_P = E_L$$

$$W_{\text{Delta}} = 3(E_L^2) / R$$

$$W_{\text{delta}} = 1.73 E_L I_L$$

Delta Connection

- Ends of the coils are connected together
- No current flows in the phase windings until a load is connected because the sum of the voltages on any two of the phases is equal and opposite to the other phase
- Line voltage is equal to the Phase voltage

$$E_L = E_P$$

- Line current is not equal to Phase current because each line carries current from two phases and are 120° out of phase

$$I_L = (1.732)(I_P)$$

- There is no neutral

Question 18

A three-phase voltage source has a voltage of 120 volts at 0 degrees and supplies a delta-connected load that has an impedance of 60 ohms at 53 degrees per phase. Calculate phase and line currents

$$I_P = \frac{E_P}{Z} = \frac{120V\angle 0^\circ}{60\Omega\angle 53^\circ} = 2A\angle -53^\circ$$

$$I_L = \sqrt{3}I_P = \sqrt{3}(2A\angle -53^\circ) = 3.5A\angle -53^\circ$$

Wye or Delta Connection

- The power that is dissipated by each phase of either a delta **or** wye connected load is:

Power per phase (P_p):

$$P_p = (E_p I_p) \cos \theta \text{ or } P_p = \frac{(E_L I_L) \cos \theta}{\sqrt{3}}$$

3 \emptyset Power ($P_{3\emptyset}$):

$$P_{3\emptyset} = 3P_p \text{ or } P_{3\emptyset} = \sqrt{3} E_L I_L \cos \theta$$

Question 19

A three-phase voltage source has a voltage of 120 volts at an angle of 0 degrees and supplies a delta connected load. Phase current is 2 amps at an angle of -53 degrees. Find the (a) power consumed per phase and (b) the total power

$$\text{a) } P_P = E_P I_P \cos \theta = (120)(2) \cos 53^\circ = 144.4 \text{ W}$$

$$\text{b) } P_{\text{Total}} = 3(P_P) = 3(144.4 \text{ W}) = 433.2 \text{ W}$$

Question 20

A three-phase generator has a phase voltage of 120 volts at 0 degrees and supplies a wye connected load. The line current is 2.4 amps at 25 degrees. Determine (a) the power dissipated by each phase, and (b) the total real power

$$\text{a) } P_P = E_P I_P \cos \theta = (120)(2.4) \cos 25^\circ = 261 \text{ W}$$

$$\text{b) } P_{\text{Total}} = 3(P_P) = 3(261 \text{ W}) = 783 \text{ W}$$

Question 21

A balanced delta load consists of (3) 20 ohm impedances at 25 degrees with a line voltage of 208 volts at 0 degrees. Find (a) phase current, (b) line current, (c) phase voltage, (d) power consumed per phase, and (e) total real power

Question 21 Answer

$$\text{a) } I_{\text{Phase}} = \frac{E_{\text{Phase}}}{R} = \frac{208 \text{ volts}}{20\Omega} = 10.4 \text{ amps}$$

$$\text{b) } I_{\text{Line}} = \sqrt{3} I_{\text{Phase}} = \sqrt{3}(10.4 \text{ amps}) = 18.01 \text{ amps}$$

$$\text{c) } E_{\text{Phase}} = E_{\text{Line}} = 208 \text{ volts}$$

$$\text{d) } P_{\text{Phase}} = E_{\text{Phase}} I_{\text{Phase}} \cos\theta = (208 \text{ volts})(10.4 \text{ amps}) \cos 25^\circ = 1961 \text{ watts}$$

$$\text{e) } P_{3\text{Phase}} = \sqrt{3} E_{\text{Line}} I_{\text{Line}} \cos\theta = \sqrt{3}(208 \text{ volts})(18.01 \text{ amps}) \cos 25^\circ = 5881 \text{ watts}$$

$$\text{Check : } P_{3\text{Phase}} = (3)P_{\text{Phase}} = (3)(1961 \text{ watts}) = 5883 \text{ watts}$$

Question 22

A balanced wye load consists of (3) 5 ohm impedances at 53.12 degrees with a line voltage of 110 volts at 0 degrees. Find the phase voltage, line current, phase current, and total real power

$$(a) E_P = \frac{E_L}{\sqrt{3}} = \frac{110}{\sqrt{3}} = 63.5 \text{ V}$$

$$b) I_L = I_P = \frac{E_P}{R} = \frac{63.5V}{5\Omega} = 12.7 \text{ A}$$

$$c) P_{3\text{-Phase}} = \sqrt{3} (E_L)(I_L) \cos(\theta) = \sqrt{3} (110)(12.7) \cos(53) = 1452 \text{ W}$$

Summary

- Identified the characteristics of Sine Waves
- Discussed the principles of AC Voltage, Current, and Phase Relations
- Computed the Energy and Power on AC Systems
- Identified Three-Phase Power and its configurations

Questions?

LabVolt Exercises

- Do LabVolt exercises 6.1 and 6.2

Disclaimer:

PJM has made all efforts possible to accurately document all information in this presentation. The information seen here does not supersede the PJM Operating Agreement or the PJM Tariff both of which can be found by accessing:

<http://www.pjm.com/documents/agreements/pjm-agreements.aspx>

For additional detailed information on any of the topics discussed, please refer to the appropriate PJM manual which can be found by accessing:

<http://www.pjm.com/documents/manuals.aspx>